


Computer Architecture

05. MIPS单周期微架构

Jianhua Li

College of Computer and Information
Hefei University of Technology

CPU中的状态元素

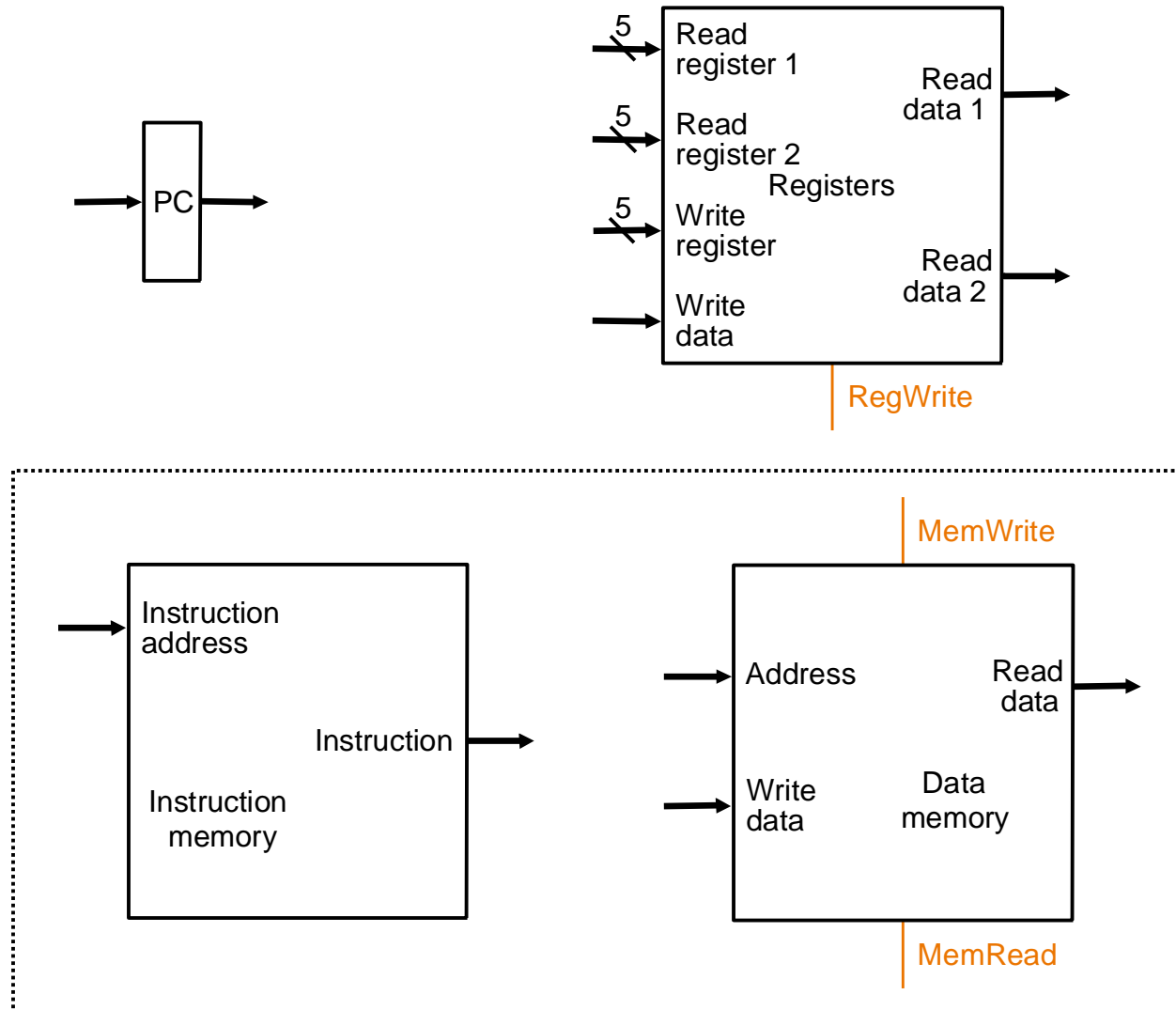


一些假设 (not practical)


- “Magic” memory and register file
- Combinational read
 - output of the read data port is a **combinational function** of the register file contents and the corresponding read select port
- Synchronous write
 - the selected register is updated on the positive edge clock transition when write enable is asserted
 - Cannot affect read output in between clock edges
- Single-cycle, synchronous memory
 - Contrast this with memory that tells when the data is ready
 - i.e., Ready bit: indicating the read or write is done

MIPS的指令处理过程

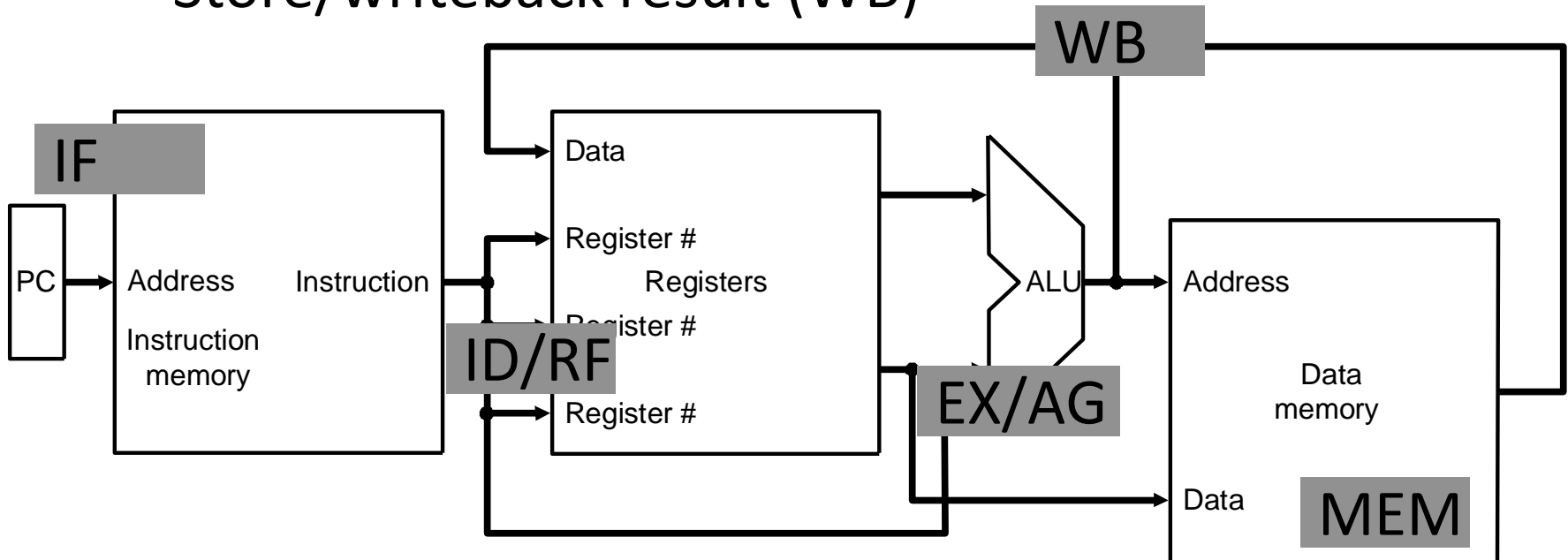- 5 generic steps
 - Instruction fetch (IF)
 - Instruction decode and register operand fetch (ID/RF)
 - Execute/Evaluate memory address (EX/AG)
 - Memory operand fetch (MEM)
 - Store/writeback result (WB)



完整的MIPS数据通路

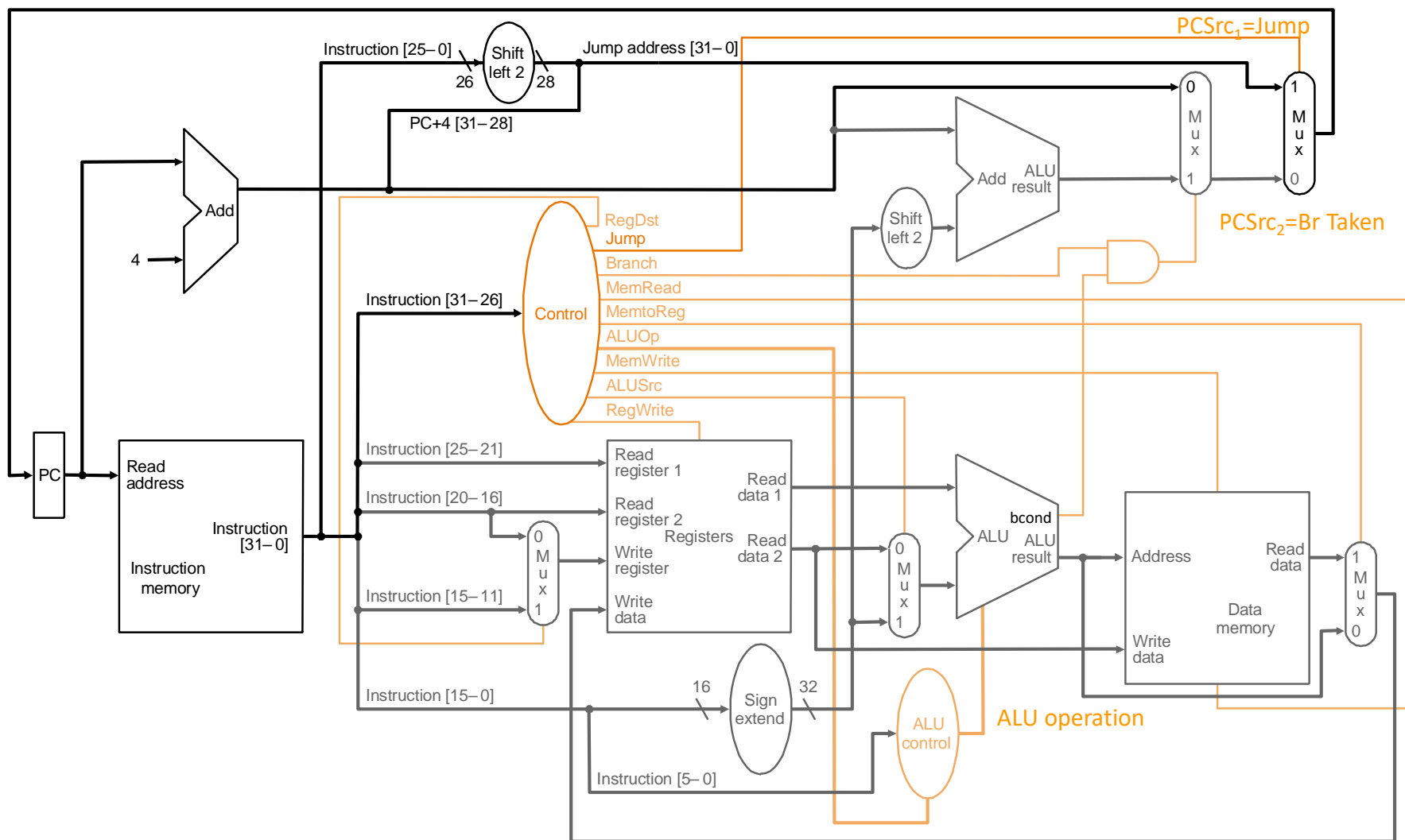

JAL, JR, JALR omitted


算术和逻辑指令的 单周期数据通路

R-Type ALU Instructions

- Assembly (e.g., register-register signed addition)

ADD rd_{reg} rs_{reg} rt_{reg}


- Machine encoding

 

- Semantics

if MEM[PC] == ADD rd rs rt
 $GPR[rd] \leftarrow GPR[rs] + GPR[rt]$
 $PC \leftarrow PC + 4$

ALU Datapath

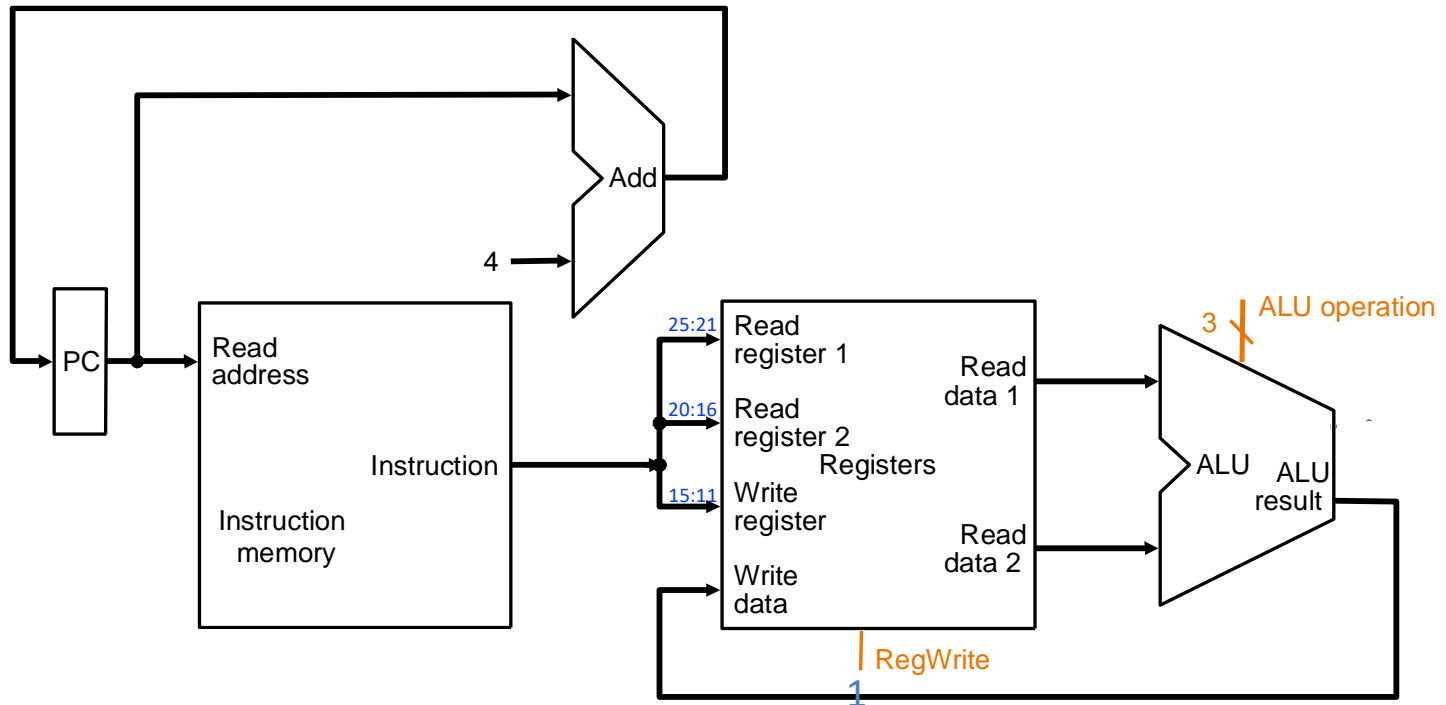

if MEM[PC] == ADD rd rs rt
GPR[rd] \leftarrow GPR[rs] + GPR[rt]
PC \leftarrow PC + 4




Combinational
state update logic

I-Type ALU Instructions

- Assembly (e.g., register-immediate signed additions)

ADDI rt_{reg} rs_{reg} immediate₁₆

- Machine encoding

 

I-type


- Semantics

if MEM[PC] == ADDI rt rs immediate

$GPR[rt] \leftarrow GPR[rs] + \text{sign-extend}(\text{immediate})$

$PC \leftarrow PC + 4$

Datapath for R and I-Type ALU Insts.

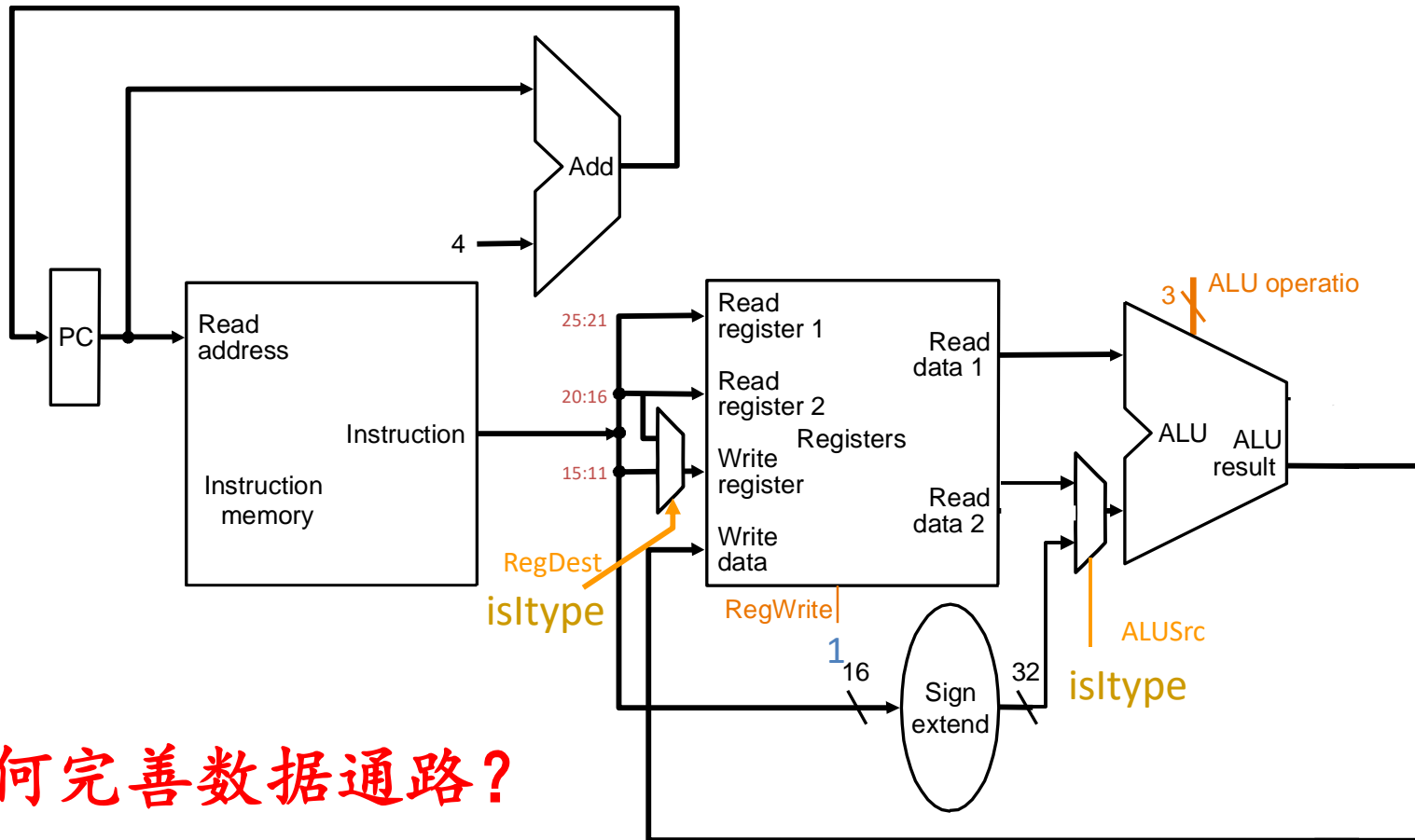

如何完善数据通路?



if MEM[PC] == ADDI rt rs immediate
 $GPR[rt] \leftarrow GPR[rs] + \text{sign-extend}(\text{immediate})$
 $PC \leftarrow PC + 4$



Combinational
state update logic


数据转移指令的 单周期数据通路

Load Instructions

- Assembly (e.g., load 4-byte word)

LW rt_{reg} $offset_{16}$ ($base_{reg}$)

- Machine encoding

 

I-type

- Semantics

if MEM[PC]==LW rt $offset_{16}$ ($base$)


EA = sign-extend(offset) + GPR[base]

GPR[rt] \leftarrow MEM[translate(EA)]

PC \leftarrow PC + 4

LW数据通路


如何完善数据通路?

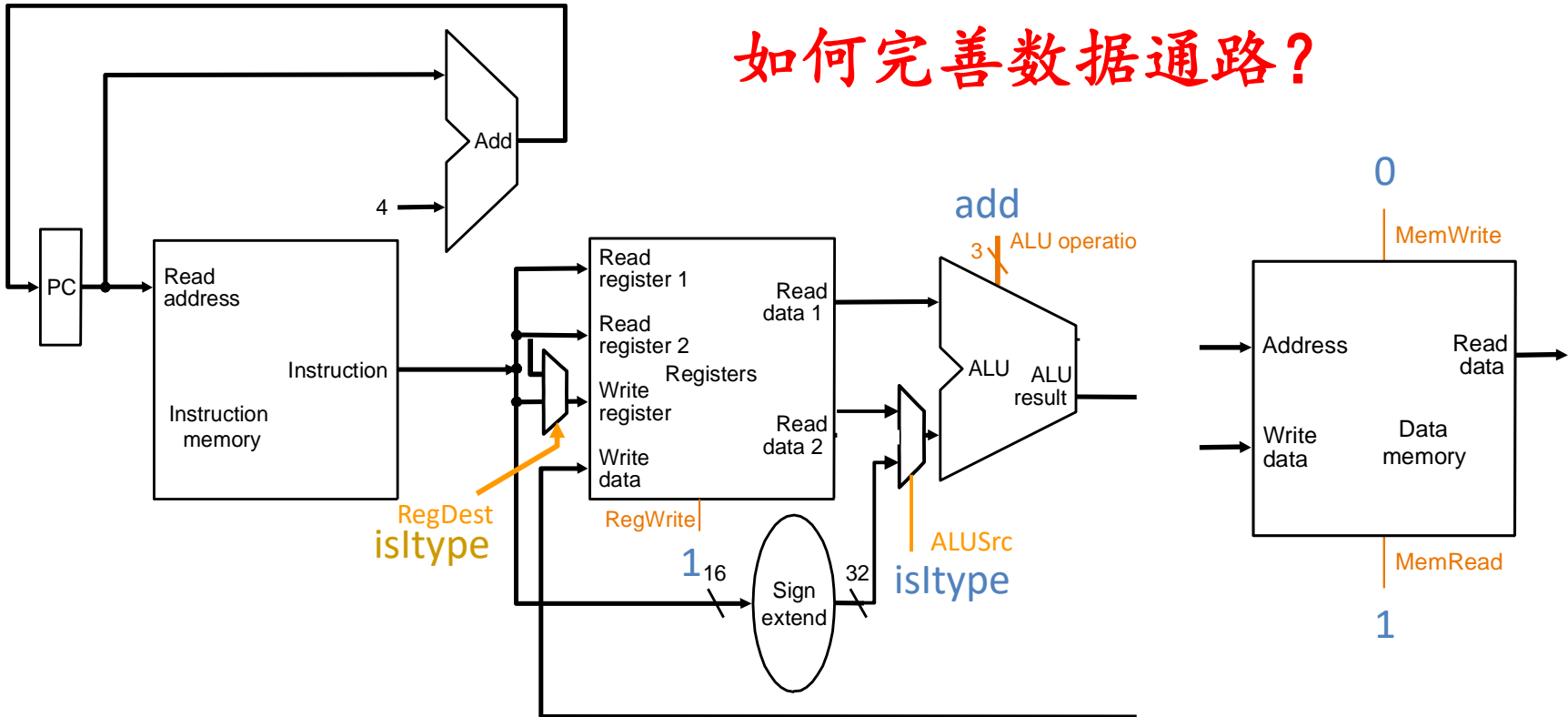

```

if MEM[PC]==LW rt offset16 (base)
    EA = sign-extend(offset) + GPR[base]
    GPR[rt] ← MEM[ translate(EA) ]
    PC ← PC + 4

```

 


Store Instructions

- Assembly (e.g., store 4-byte word)

$SW\ rt_{reg}\ offset_{16}\ (base_{reg})$

- Machine encoding

 

I-type

- Semantics

$if\ MEM[PC] == SW\ rt\ offset_{16}\ (base)$


$EA = \text{sign-extend}(\text{offset}) + GPR[\text{base}]$

$MEM[\text{translate}(EA)] \leftarrow GPR[rt]$

$PC \leftarrow PC + 4$

SW数据通路

如何完善数据通路？

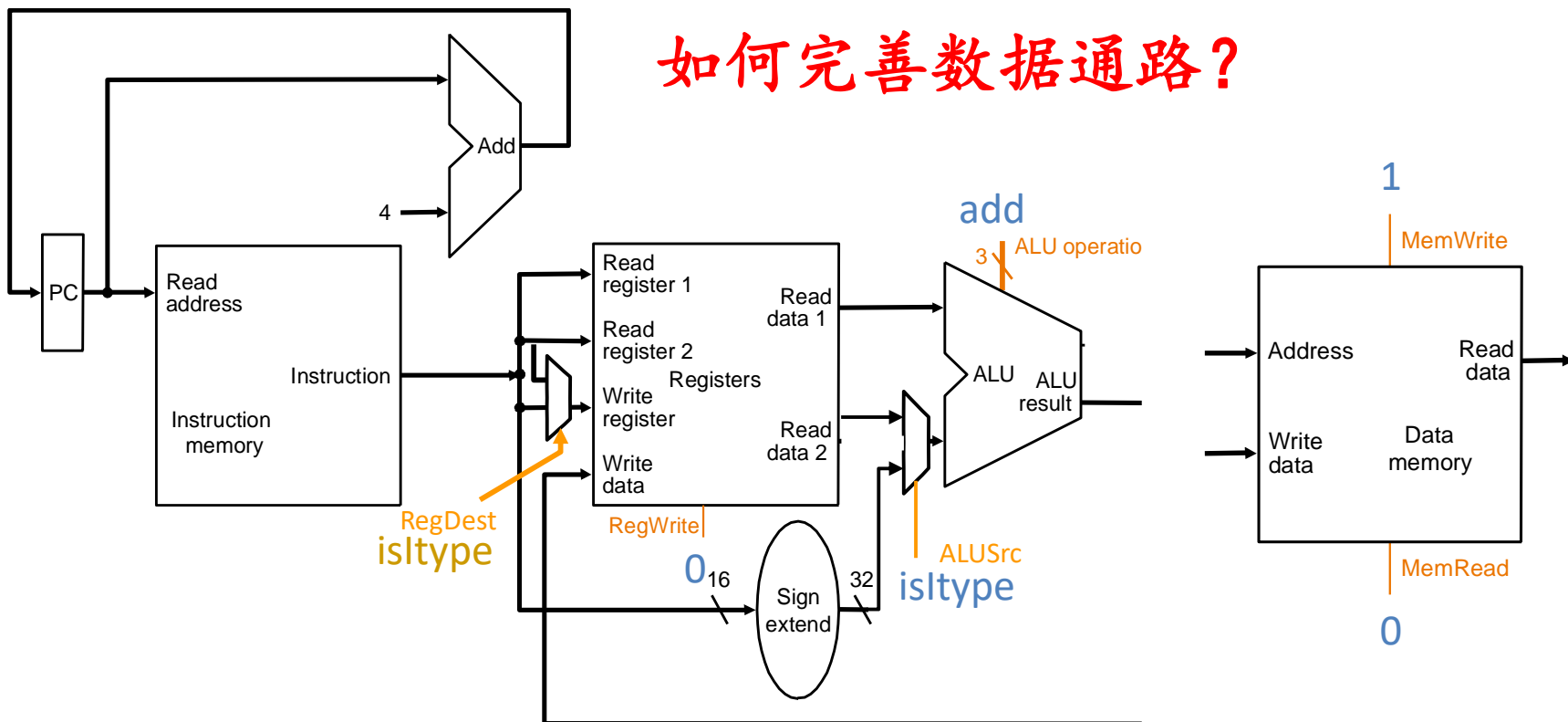


if $\text{MEM}[\text{PC}] == \text{SW rt offset}_{16}(\text{base})$
 $\text{EA} = \text{sign-extend}(\text{offset}) + \text{GPR}[\text{base}]$
 $\text{MEM}[\text{translate}(\text{EA})] \leftarrow \text{GPR}[\text{rt}]$
 $\text{PC} \leftarrow \text{PC} + 4$

IF	ID	EX	MEM	WB
----	----	----	-----	----




Combinational
state update logic

Load-Store数据通路

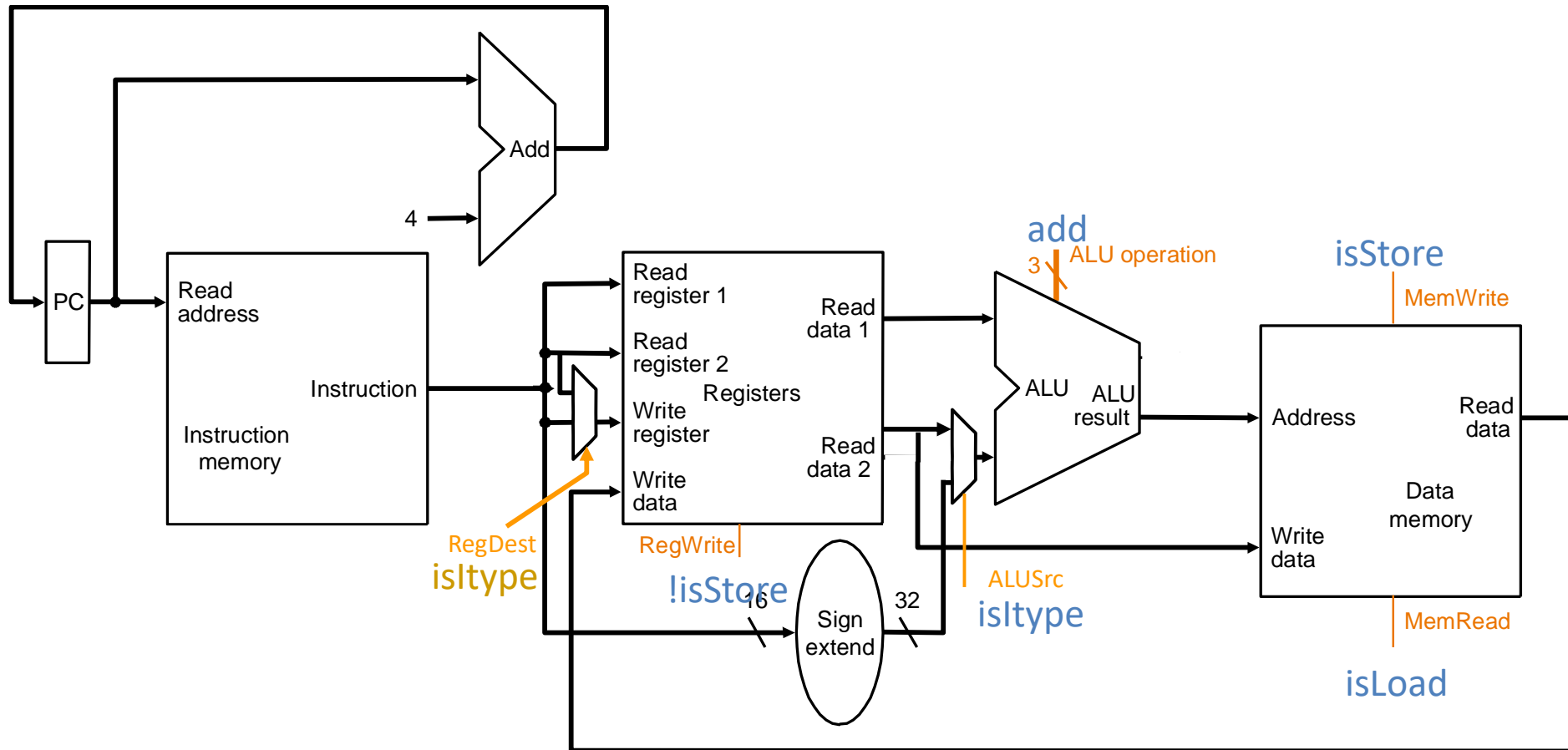

非控制流指令的数据通路

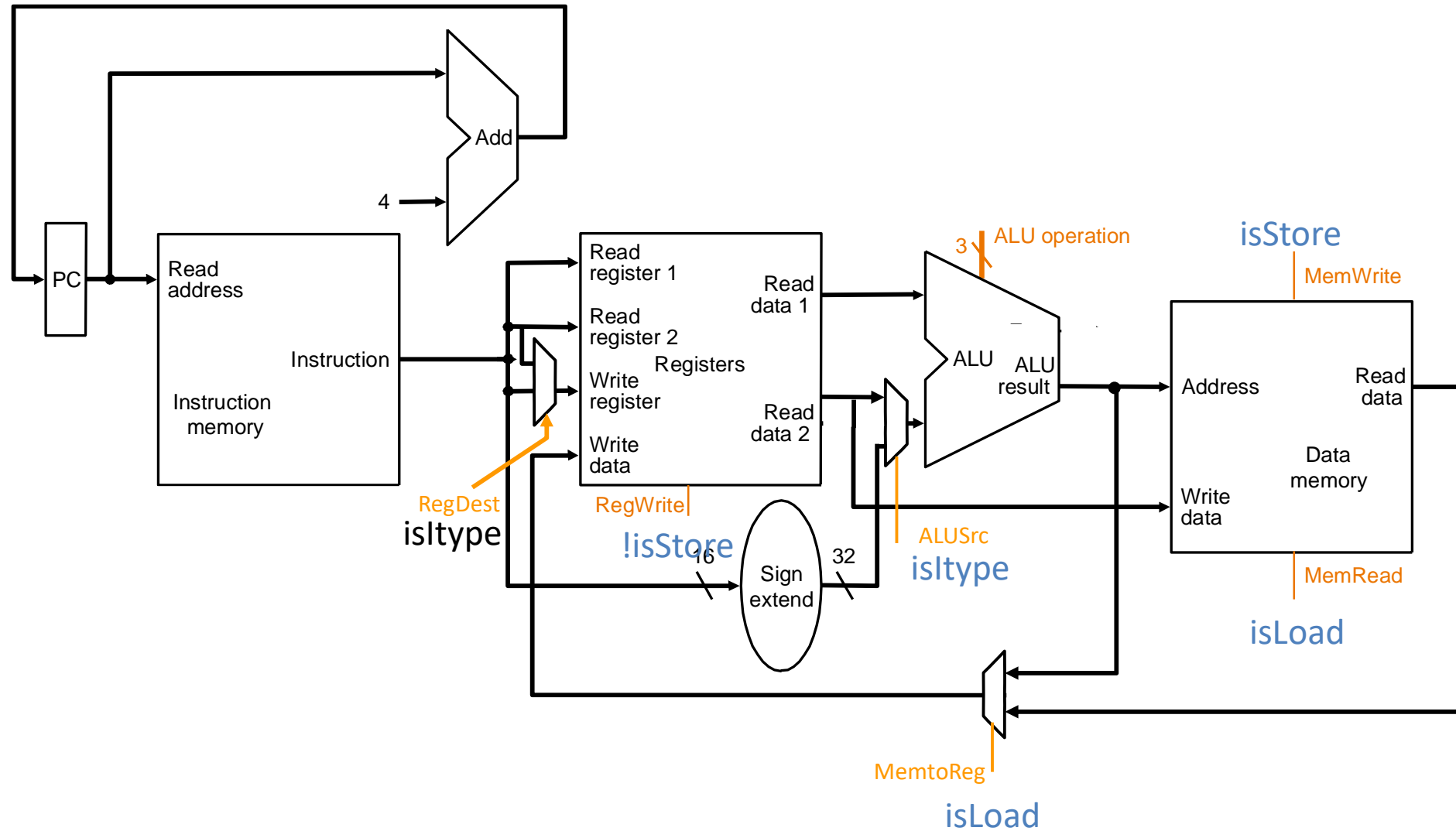


控制流指令的 单周期数据通路

无条件跳转指令

- Assembly

J immediate₂₆

- Machine encoding

 

J-type


- Semantics

if MEM[PC]==J immediate₂₆

target = { PC[31:28], immediate₂₆, 2' b00 }

PC ← target

无条件跳转指令的数据通路

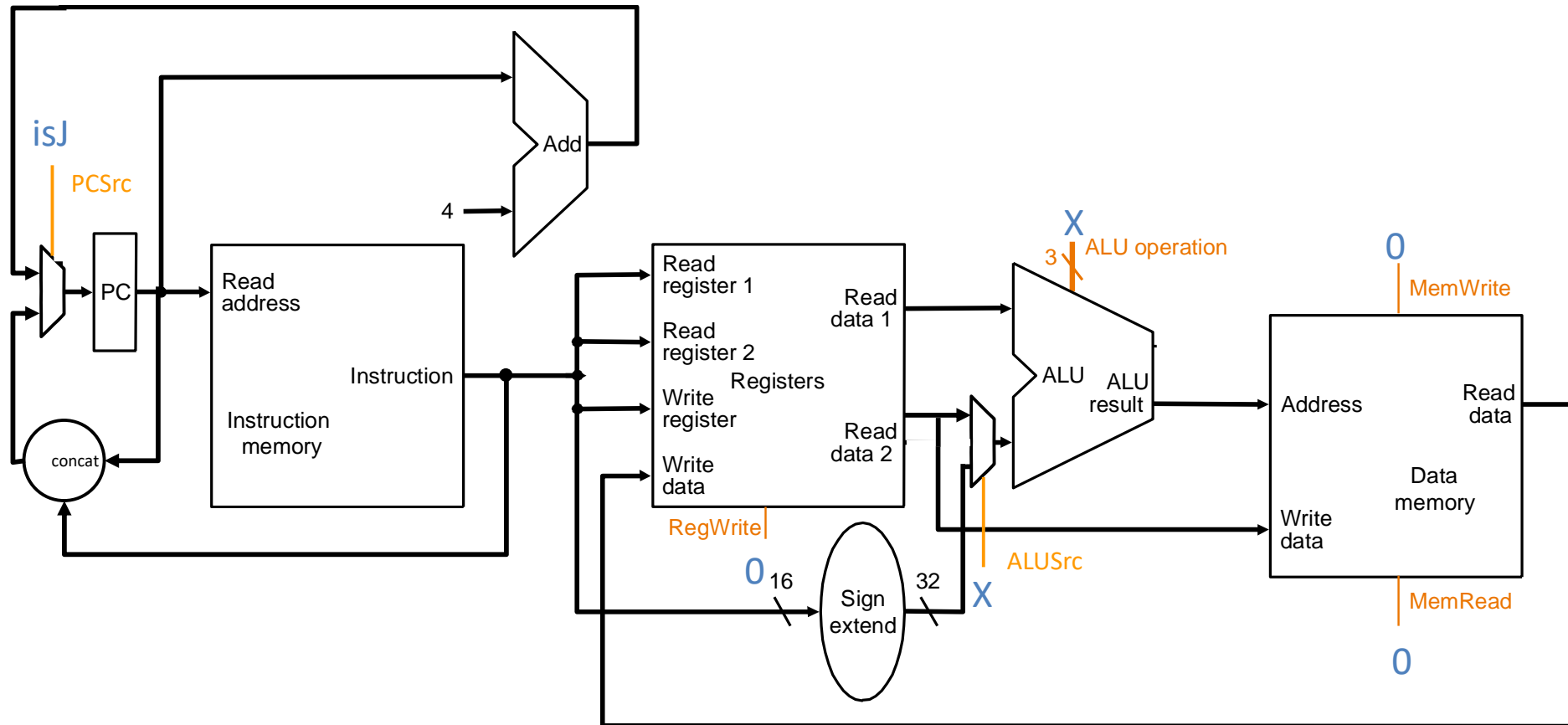

if $\text{MEM}[\text{PC}] == \text{J immediate26}$
 $\text{PC} = \{ \text{PC}[31:28], \text{immediate26}, 2' \text{ b}00 \}$


What about JR, JAL, JALR?

条件分支指令

- Assembly (e.g., branch if equal)

BEQ rs_{reg} rt_{reg} immediate₁₆

- Machine encoding

 

- Semantics (assuming no branch delay slot)


if MEM[PC]==BEQ rs rt immediate₁₆

target = PC + 4 + sign-extend(immediate) x 4


if GPR[rs]==GPR[rt] then PC ← target

else PC ← PC + 4

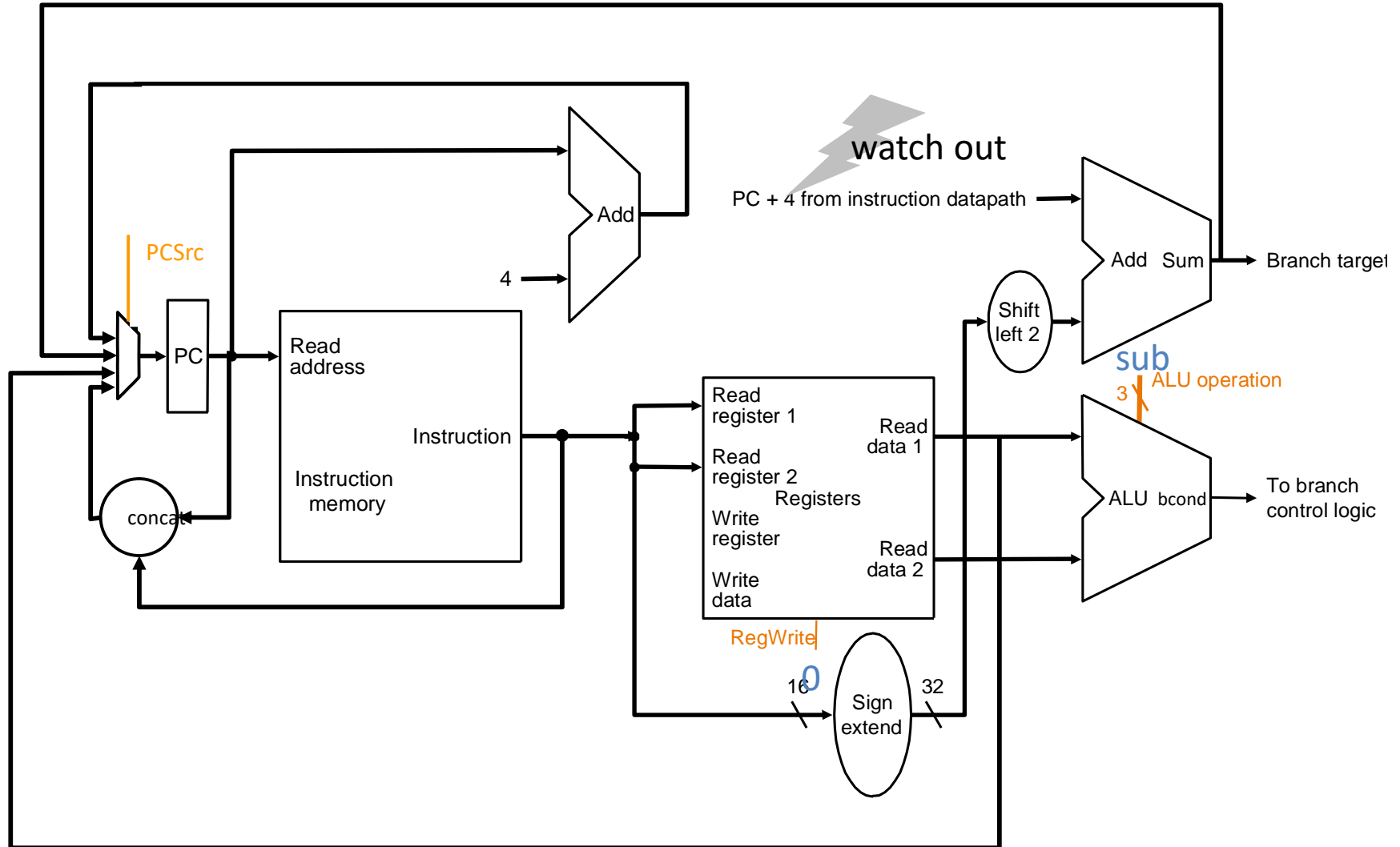Conditional Branch Datapath (for you to finish)



Putting It All Together

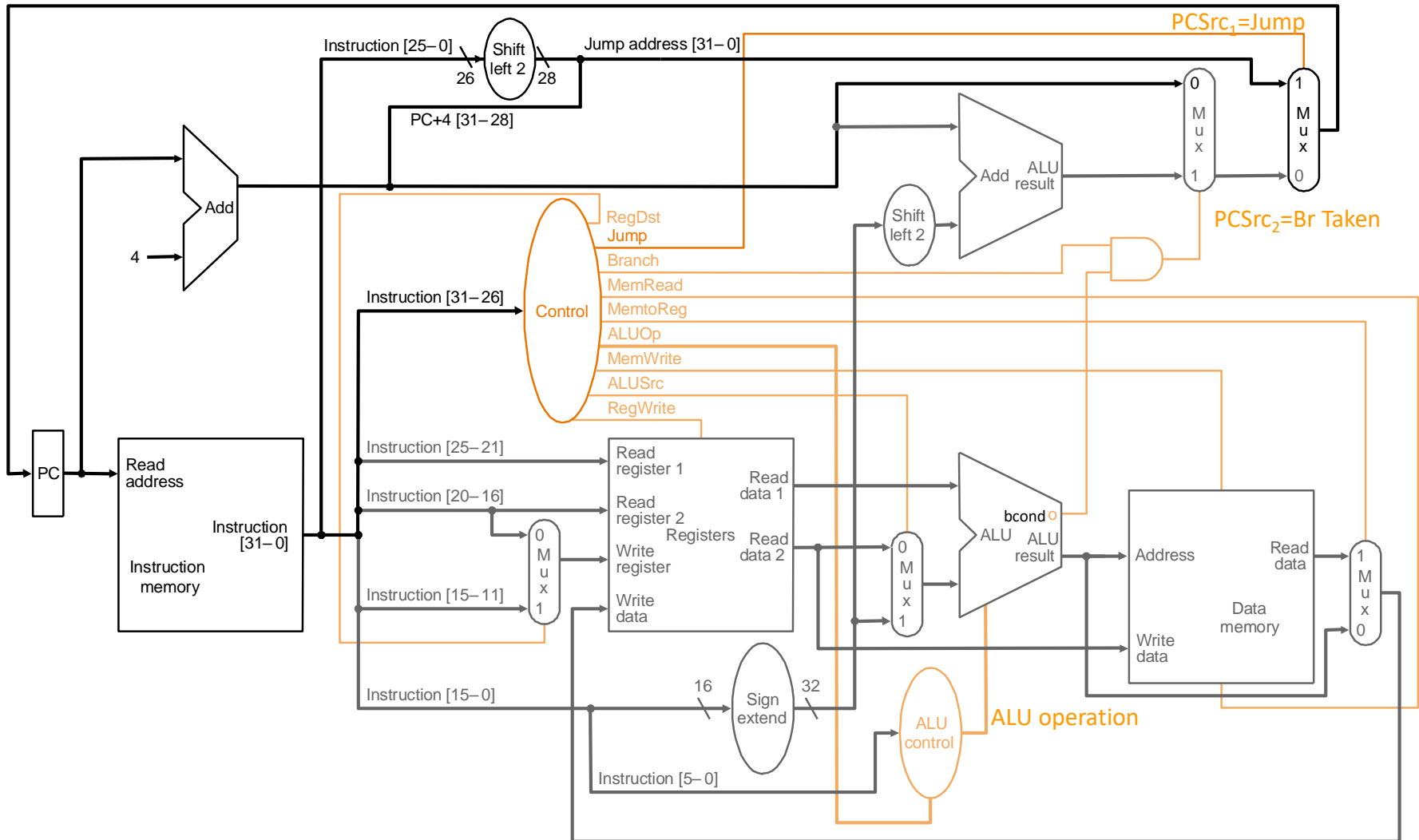


JAL, JR, JALR omitted


单周期控制逻辑

单周期硬布线控制

 
- As **combinational function** of $\text{Inst} = \text{MEM}[\text{PC}]$



R-type

 

I-type

 

J-type

- Consider
 - All R-type and I-type ALU instructions
 - LW and SW
 - BEQ, BNE, BLEZ, BGTZ
 - J, JR, JAL, JALR

单个比特控制信号

	When De-asserted	When asserted	Equation
RegDest	GPR write select according to rt , i.e., inst[20:16]	GPR write select according to rd , i.e., inst[15:11]	opcode ==0
ALUSrc	2 nd ALU input from 2 nd GPR read port	2 nd ALU input from sign-extended 16-bit immediate	(opcode !=0) && (opcode !=BEQ) && (opcode !=BNE)
MemtoReg	Steer ALU result to GPR write port	steer memory load to GPR wr. port	opcode ==LW
RegWrite	GPR write disabled	GPR write enabled	(opcode !=SW) && (opcode !=Bxx) && (opcode !=J) && (opcode !=JR))

JAL and JALR require additional RegDest and MemtoReg options

单个比特控制信号

	When De-asserted	When asserted	Equation
MemRead	Memory read disabled	Memory read port return load value	$opcode == LW$
MemWrite	Memory write disabled	Memory write enabled	$opcode == SW$
PCSrc ₁	According to PCSrc ₂	next PC is based on 26-bit immediate jump target	$(opcode == J) \vee (opcode == JAL)$
PCSrc ₂	next PC = PC + 4	next PC is based on 16-bit immediate branch target	$(opcode == Bxx) \wedge \text{“bcond is satisfied”}$

JR and JALR require additional PCSrc options

ALU Control

- case **opcode**

- ‘0’ \Rightarrow select operation according to **funct**

- ‘ALUi’ \Rightarrow selection operation according to **opcode**

- ‘LW’ \Rightarrow select addition

- ‘SW’ \Rightarrow select addition

- ‘Bxx’ \Rightarrow select bcond generation function


- __ \Rightarrow don't care

- Example ALU operations


- ADD, SUB, AND, OR, XOR, NOR, etc.

- bcond on equal, not equal, LE zero, GT zero, etc.


R-Type ALU

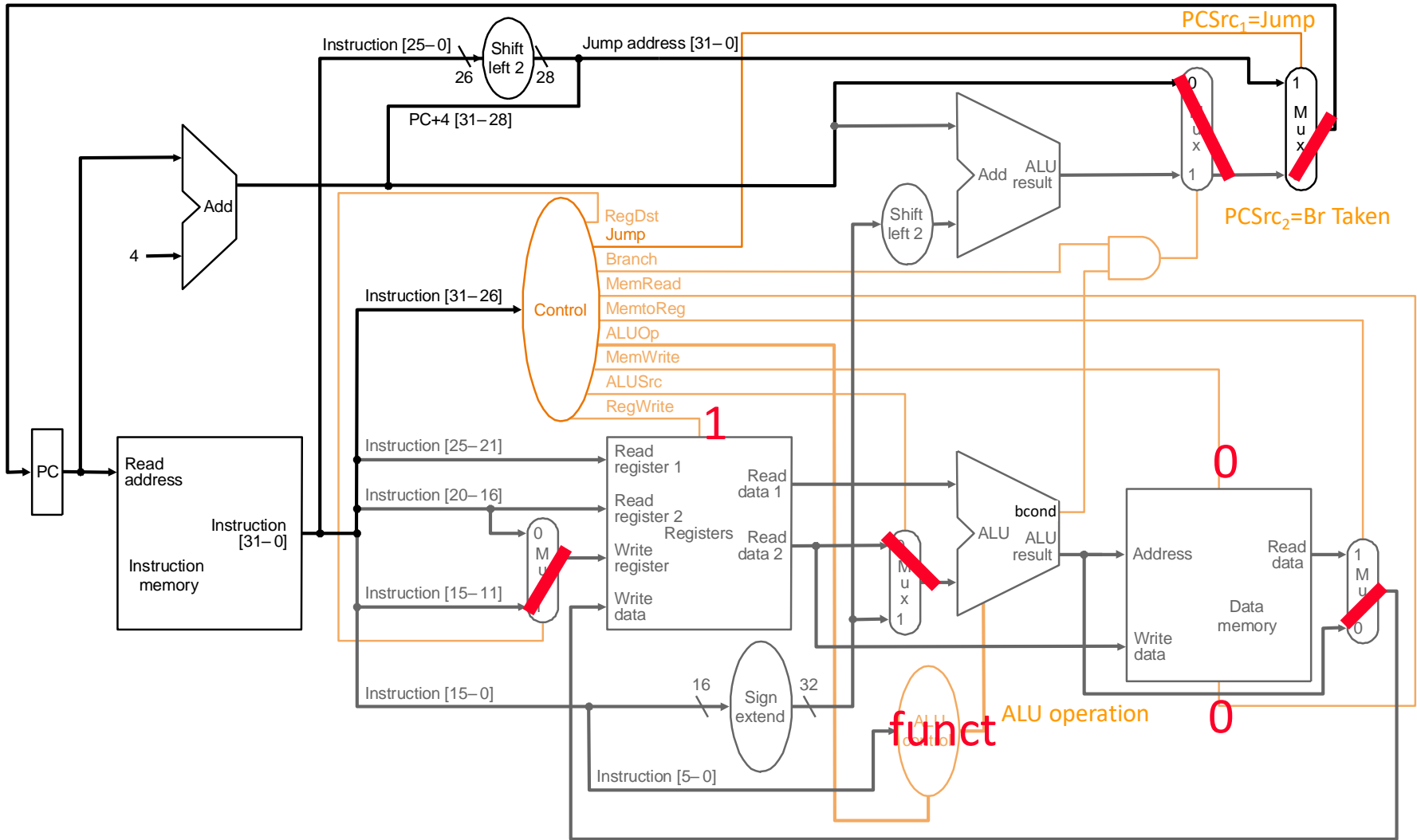


I-Type ALU

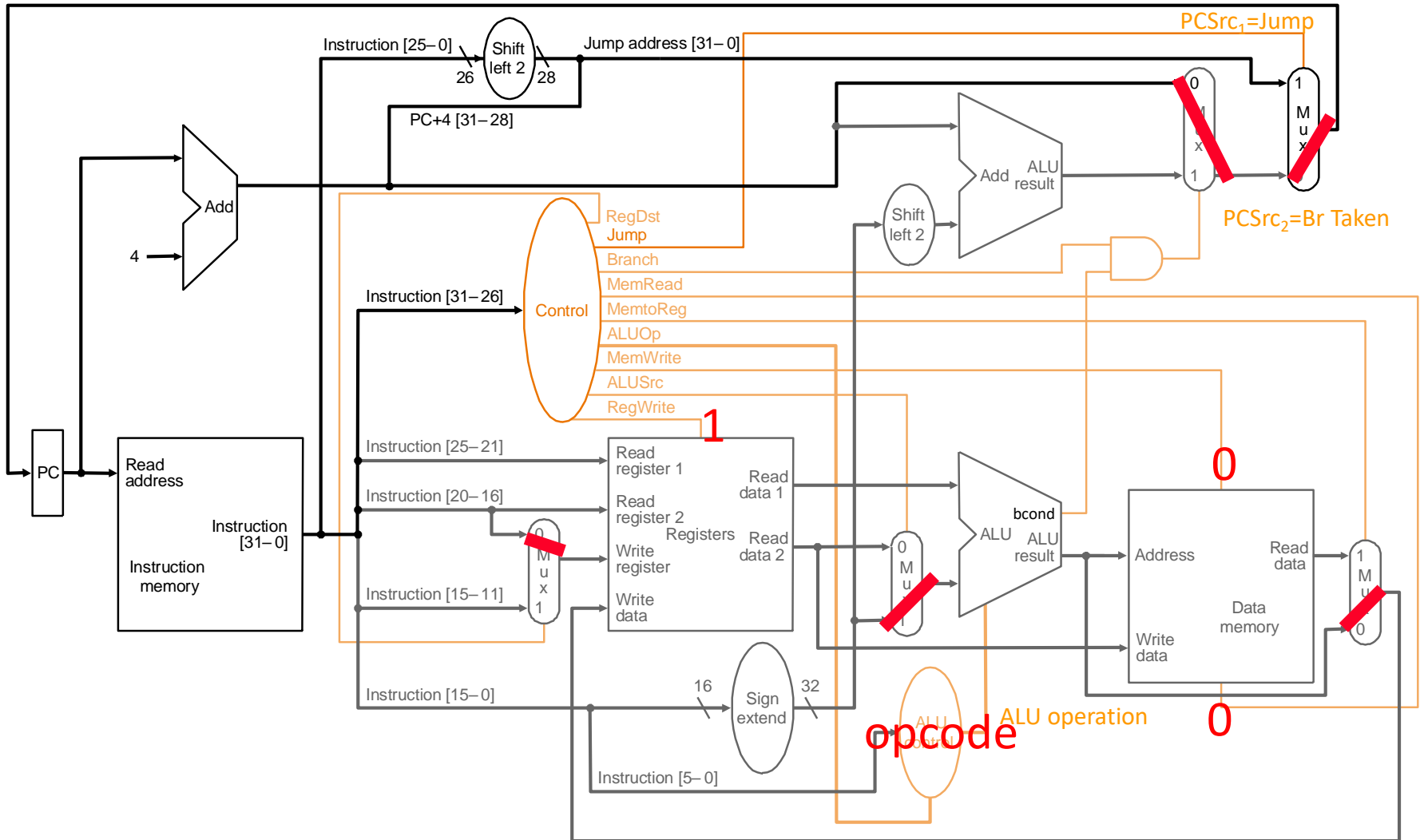

LW

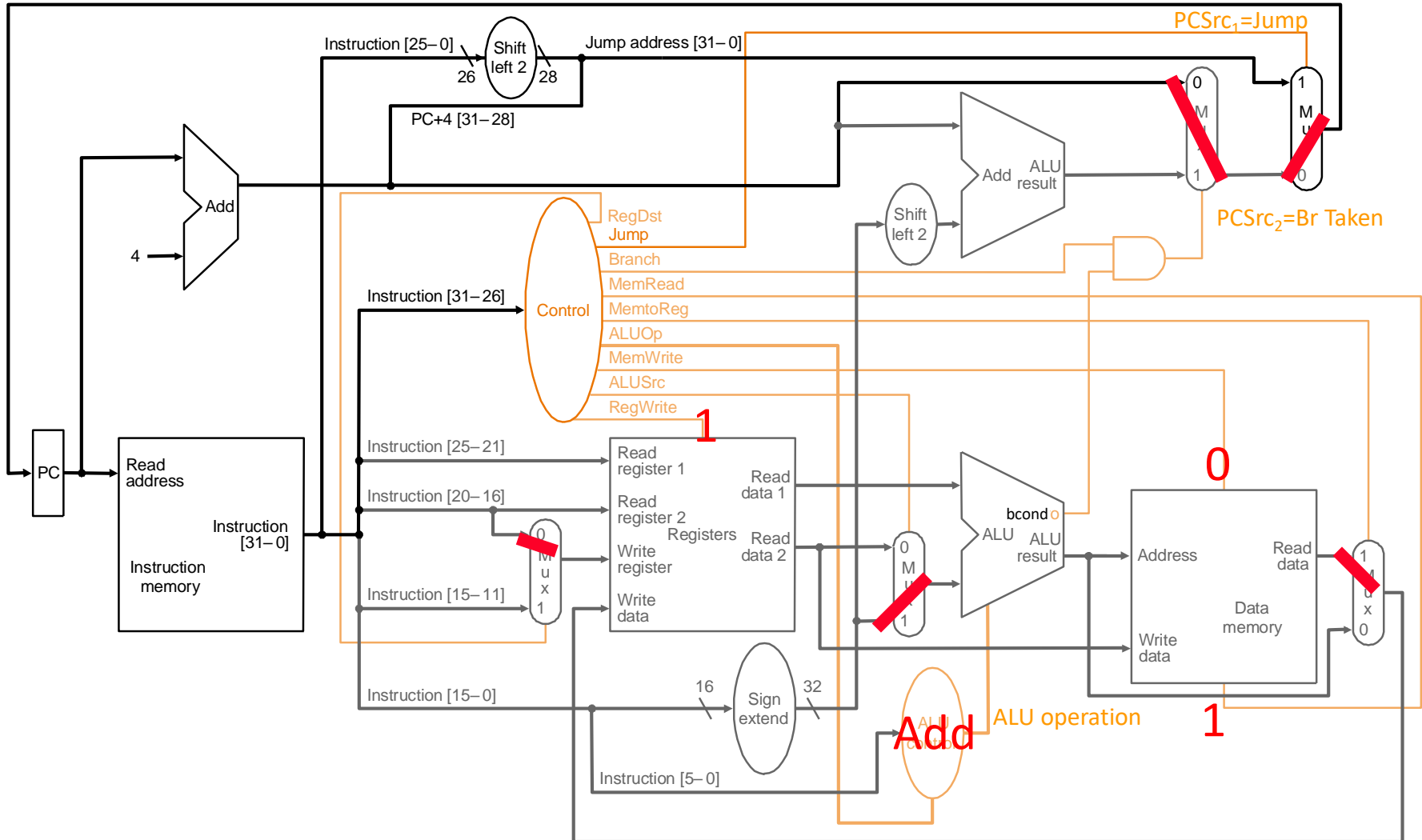


SW

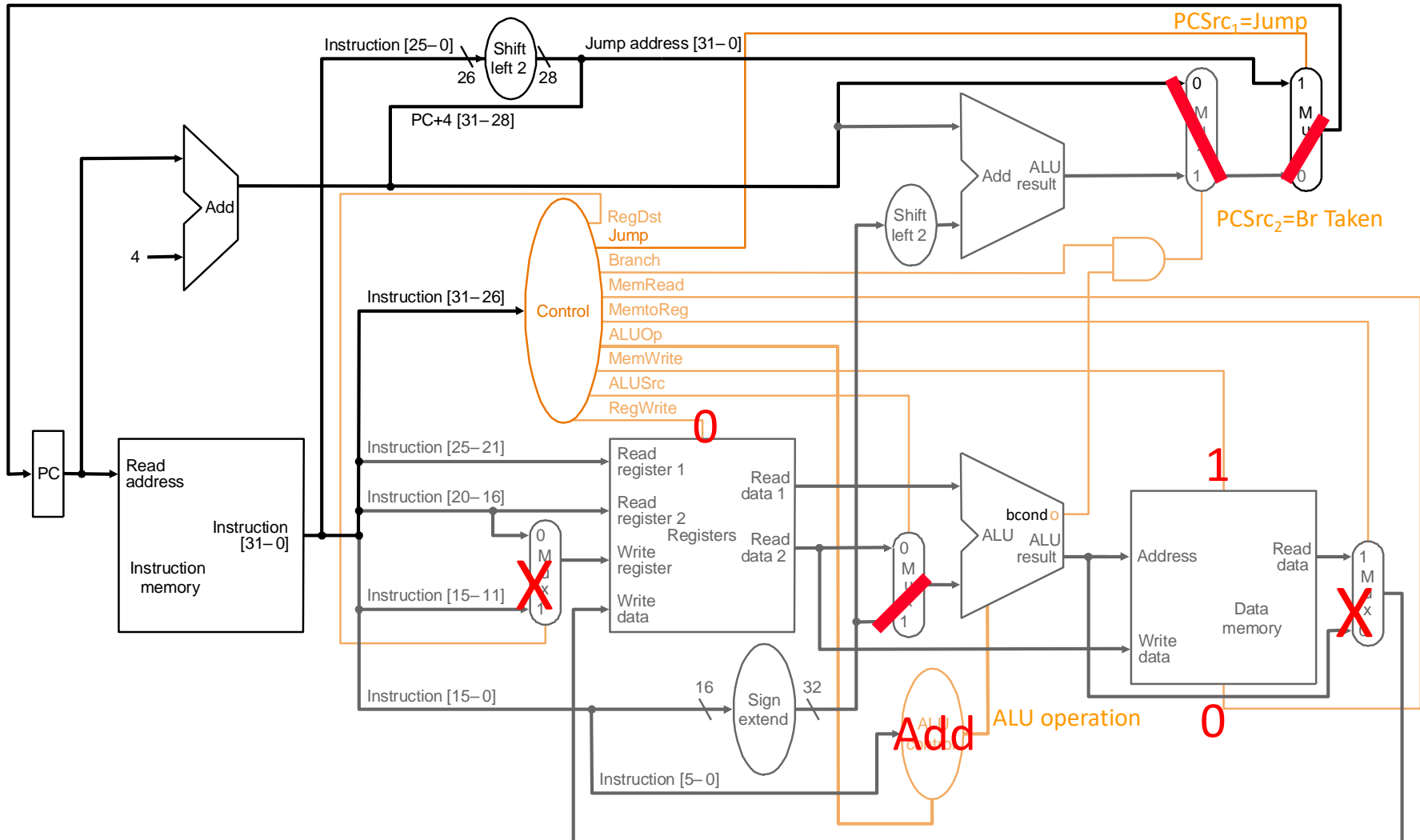


Branch (Not Taken)

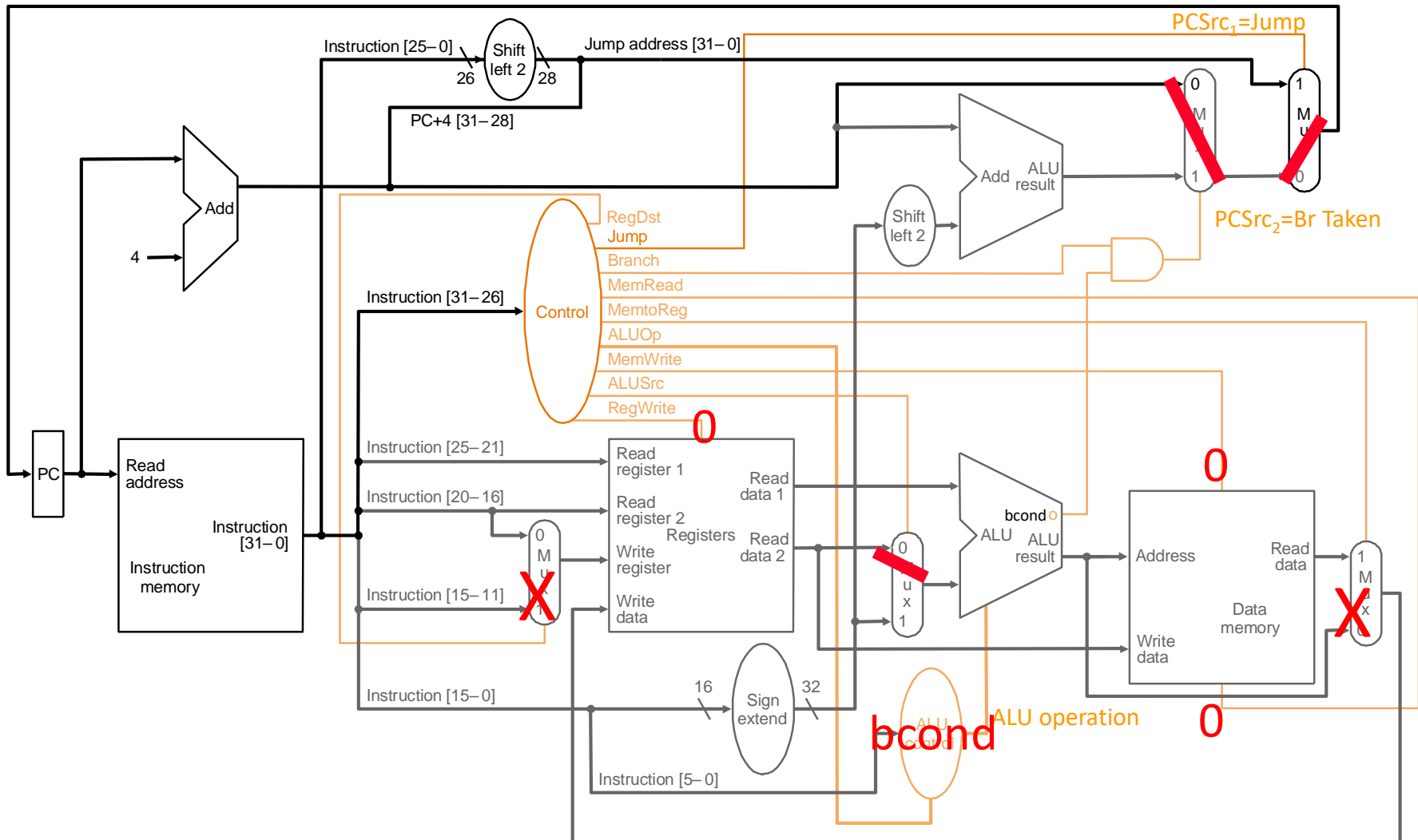Some control signals are dependent on the processing of data




Branch (Taken)

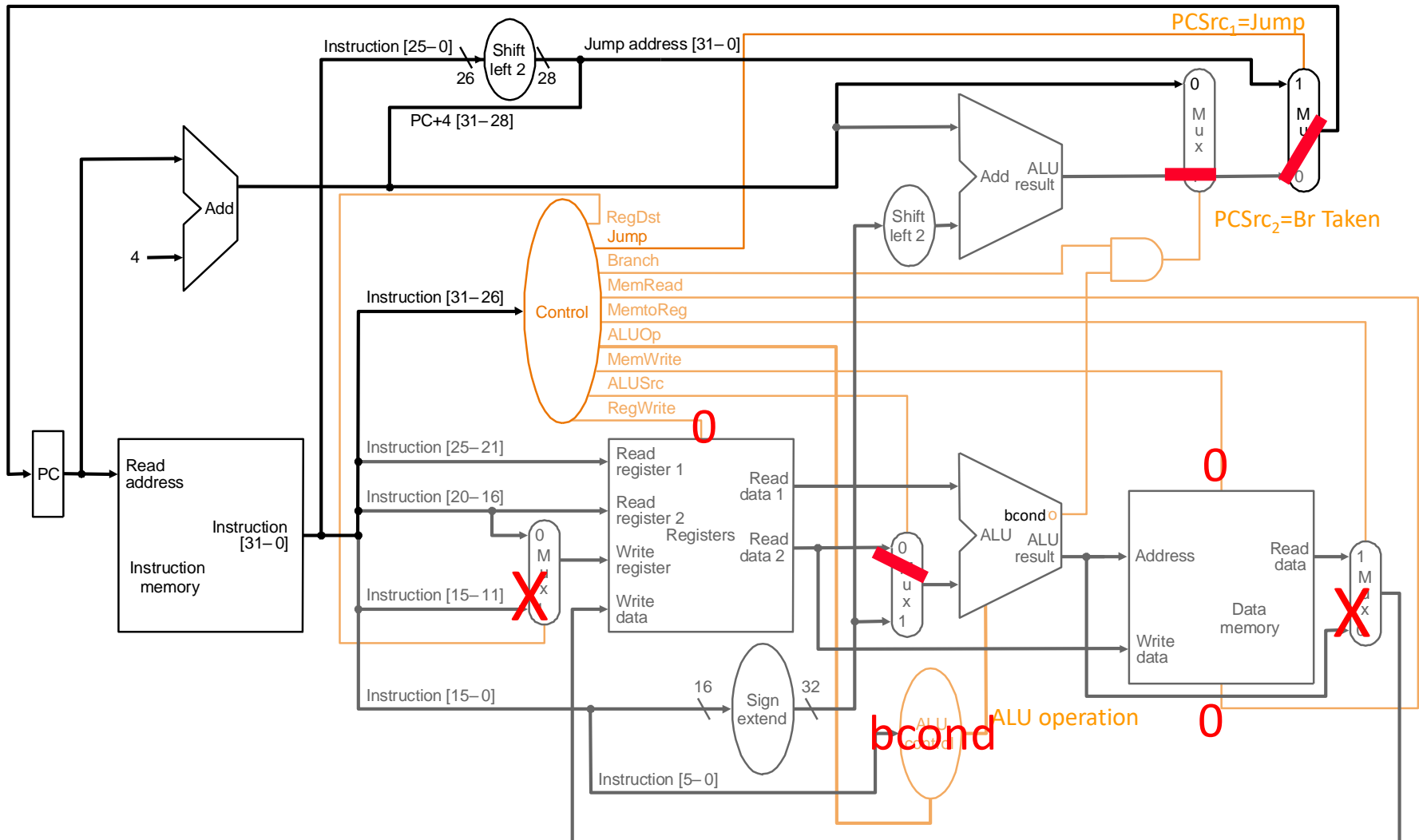Some control signals are dependent on the processing of data



Jump

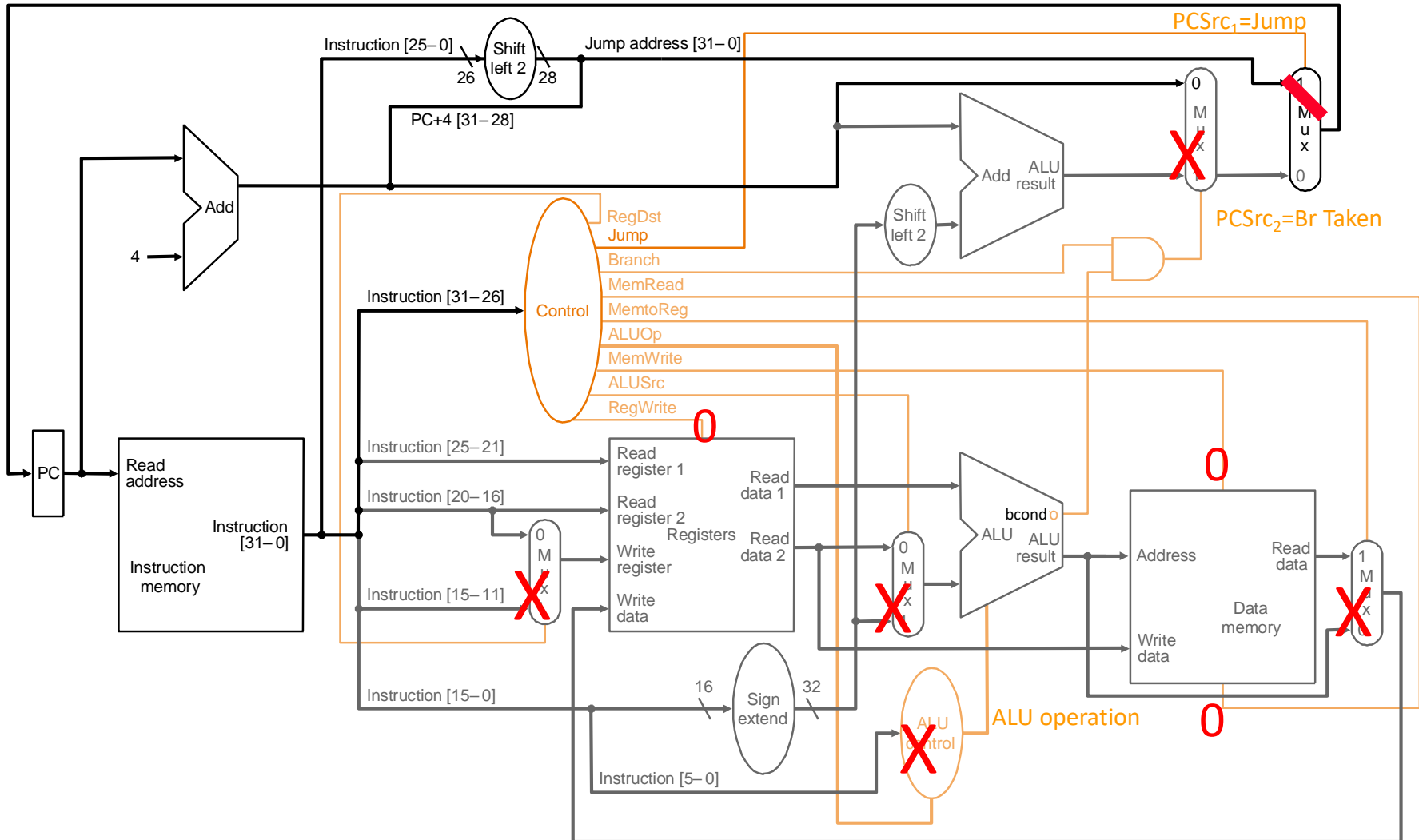

What is in the Control Box?

- Combinational Logic → **Hardwired Control**
 - Idea: Control signals generated combinatorially based on instruction
 - Necessary in a single-cycle microarchitecture...
- Sequential Logic → **Sequential/Microprogrammed Control**
 - Idea: A memory structure contains the control signals associated with an instruction
 - Control Store

MIPS单周期微架构的评测

A Single-Cycle Microarchitecture: Analysis

- Every instruction takes 1 cycle to execute
 - CPI (Cycles per instruction) is strictly 1
- How long each instruction takes is determined by how long the slowest instruction takes to execute
 - Even though many instructions do not need that long to execute
- Clock cycle time of the microarchitecture is determined by how long it takes to complete the slowest instruction
 - Critical path of the design is determined by the processing time of the slowest instruction

What is the Slowest Instruction to Process?


- Let's go back to the basics
- All five phases of the instruction processing cycle take a single machine clock cycle to complete
 - Instruction fetch (IF)
 - Instruction decode and register operand fetch (ID/RF)
 - Execute/Evaluate memory address (EX/AG)
 - Memory operand fetch (MEM)
 - Store/writeback result (WB)
- Do each of the above phases take the same time (latency) for all instructions?

单周期数据通路分析


- Assume
 - memory units (read or write): 200 ps
 - ALU and adders: 100 ps
 - register file (read or write): 50 ps
 - other combinational logic: 0 ps

steps	IF	ID	EX	MEM	WB	Delay
resources	mem	RF	ALU	mem	RF	
R-type	200	50	100		50	400
I-type	200	50	100		50	400
LW	200	50	100	200	50	600
SW	200	50	100	200		550
Branch	200	50	100			350
Jump	200					200


找出关键路径

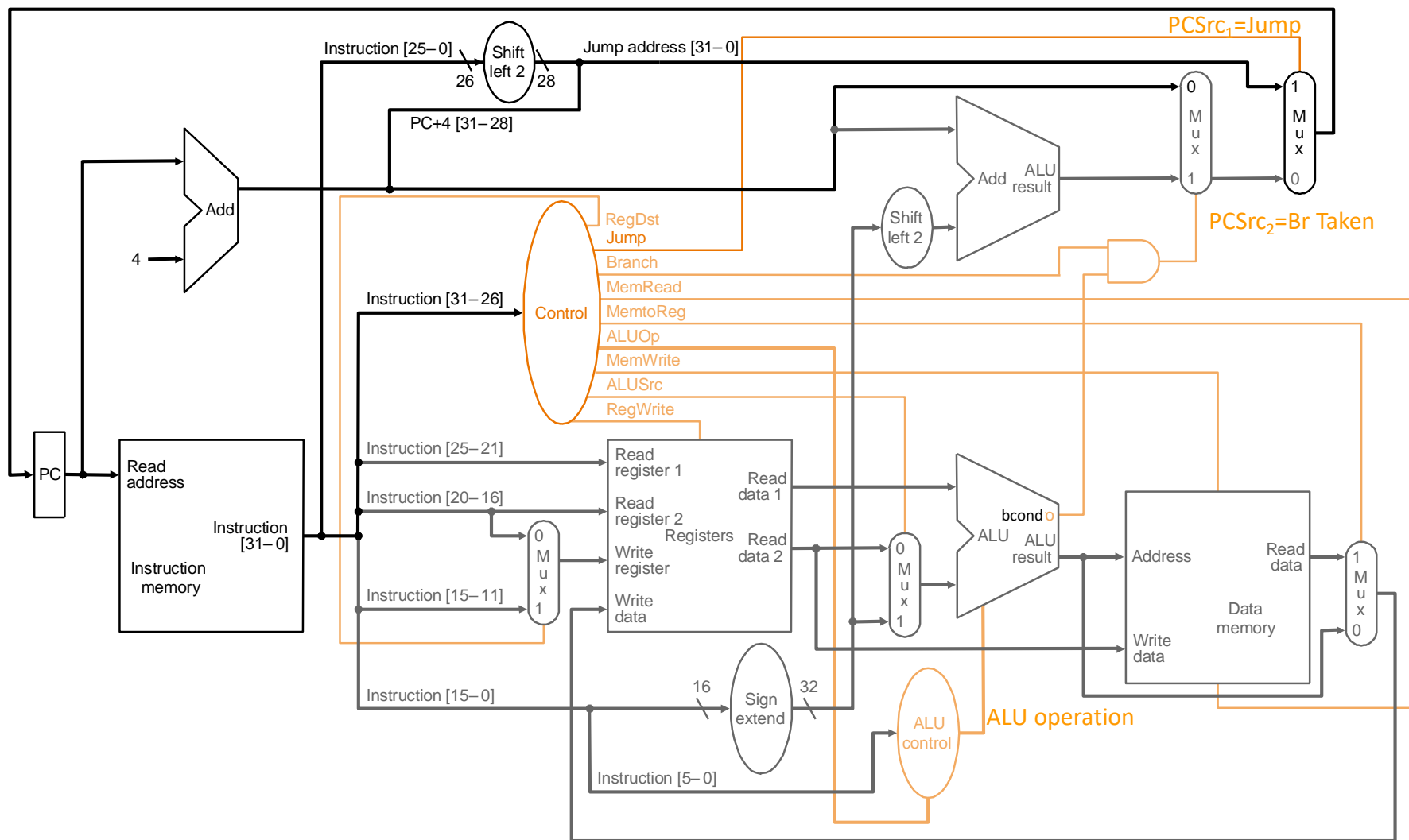


R-Type and I-Type ALU

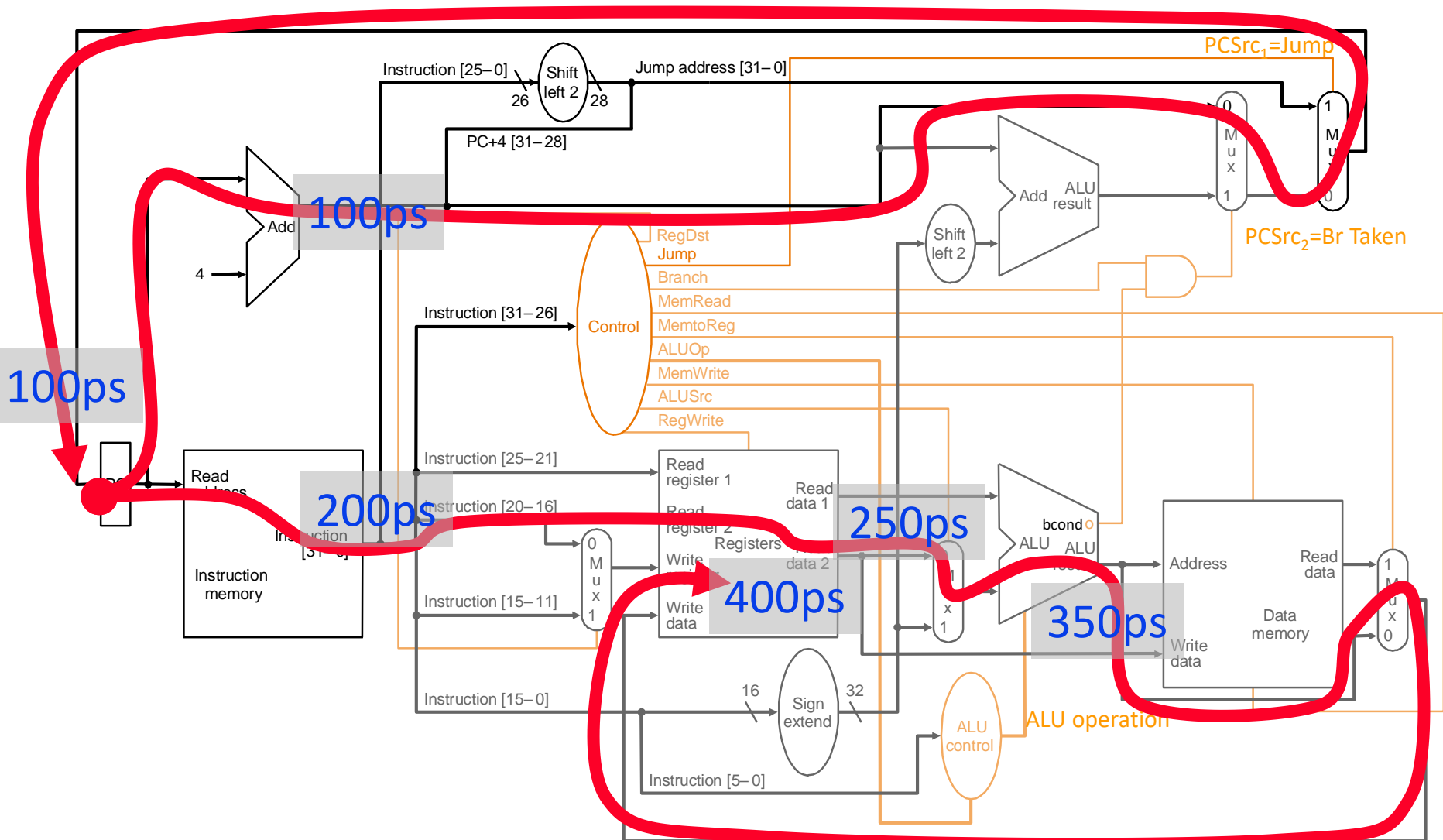


LW

 

SW

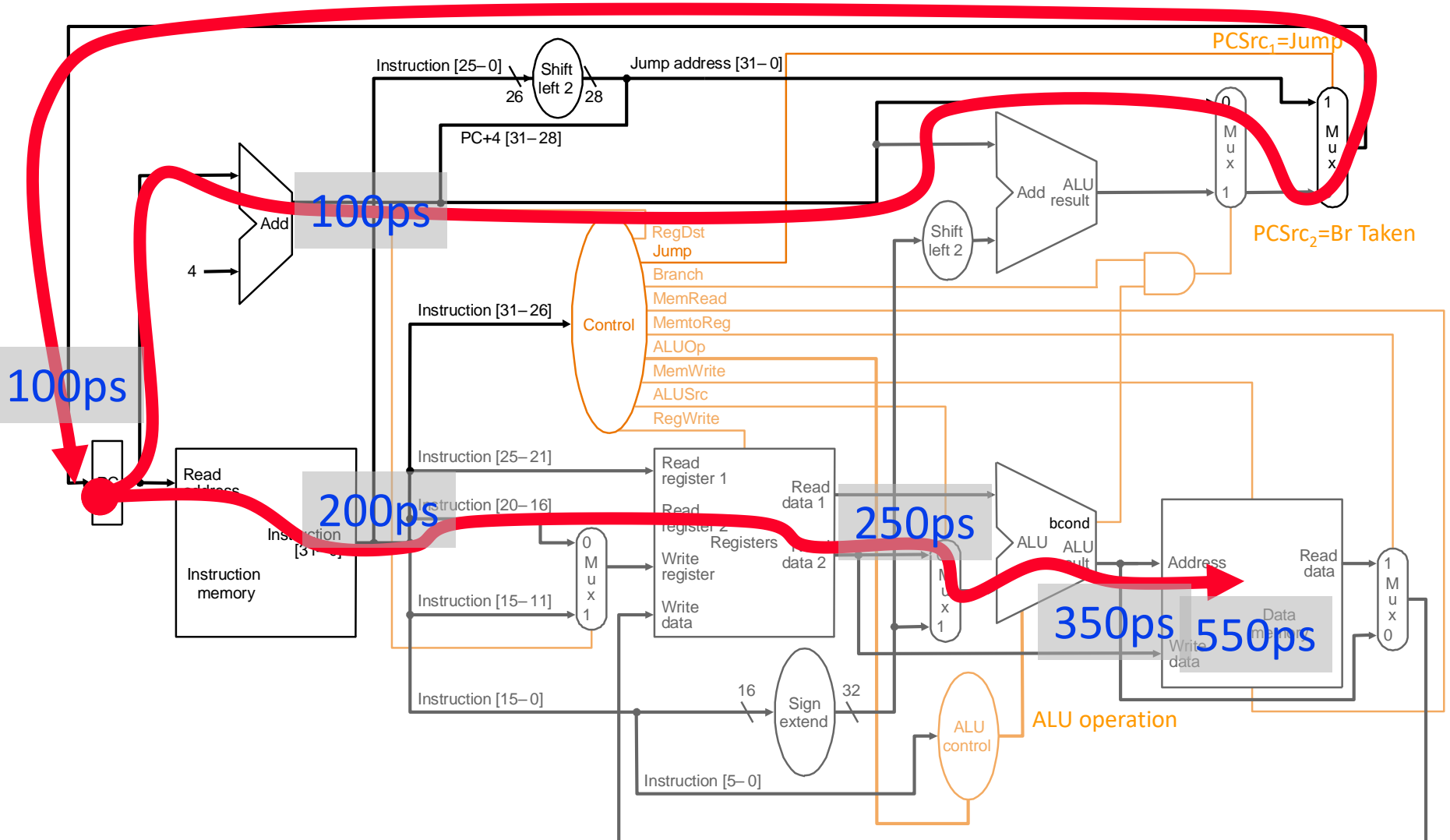

Branch Taken

 

Jump

